

PRACTICAL WORK BOOK
For Academic Session 2012

ELECTRONIC DEVICES & CIRCUITS
(EL-231) For S.E(EL)

Name: _____

Roll Number: _____

Class: _____

Batch: _____

Department : _____



Department of Electronic Engineering
NED University of Engineering & Technology, Karachi

LABORATORY WORK BOOK

FOR THE COURSE

EL -231 Electronic Devices & Circuits

Prepared By:

Ms. Madiha Shabir Shaikh (Lecturer)

Reviewed By:

Mr. Muhammad Khurram Shaikh(Assistant Professor)

Approved By:

The Board of Studies of Department of Electronic Engineering

Electronic Devices and Circuits Laboratory

CONTENTS

La b. No.	Dated	List of Experiments	Page No .	Remarks
1		To study the Operation of Inverting Operational Amplifiers	4	
2		To study the Operation of Weighted Summer using Op-amps	6	
3		To study the Operation of Inverting Integrator using Op-amps	8	
4		To study the operation of simple BJT Current Source	10	
5		To study the operation of BJT Wilson Current Mirror	12	
6		To study the operation of BJT Differential Pair	14	
7		To study the operation of MOS Widlar Current Source	16	
8		To study the operation of Common Source Amplifier	18	
9		To study the operation of Common Gate Amplifier	20	
10		PROJECT # 1 To study the operation of Instrumentation Amplifier	22	
11		PROJECT # 2 To study the operation of Cascode Amplifier	23	
12		PROJECT # 3 To study the operation of Common Drain	24	

Lab Session 01

OBJECTIVES

To investigate the Inverting Amplifier i.e.

To determine the phase shift between the input and output signals.


To measure the frequency response of an op amp and demonstrate the effect of negative feedback

EQUIPMENT REQUIRED:

Protoboard
741 Opamps
Resistors
Digital Multimeter
Function Generator
Oscilloscope

Theory:

Figure shows the inverting configuration. It consists of one opamp & two resistors R_1 & R_2 . R_2 is connected from output terminal back to inverting or inverting input terminal. If $R_2/R_1 = 10$, & we apply the sine wave input of 1V pk-pk, output will be a sine wave of 10V pk-pk, & phase shifted 180°

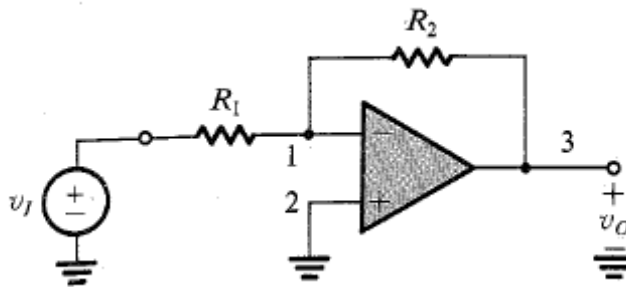

Observations:

S.No	Frequency	Input (p-p)	Output (p-p)	Gain
1	1k			
2				
3				
4				
5	10k			
6				
7				
8				
9	100k			
10				
11				
12				

Calculations:

Calculated Gain:

$$G=V_o/V_i=-(R_2/R_1)$$

Lab Session 02

OBJECTIVES

To investigate the Weighted Summer Operation


EQUIPMENT REQUIRED:

Protoboard
741 Opamps
Resistors
Digital Multimeter
Function Generator
Oscilloscope

THEORY:

Figure shows that there are number of input signals, V_1, V_2, \dots, V_n each applied to a corresponding resistor R_1, R_2, \dots, R_n , which are connected to inverting terminal of Opamp

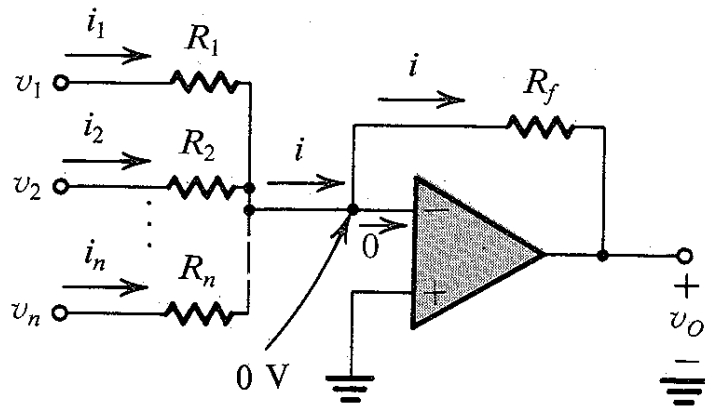Output is the weighted sum of the input signals V_1, V_2, \dots, V_n . Each summing coefficient may be independently adjusted using R_1, R_2, \dots, R_n



$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$

OBSERVATIONS:

S. No	INPUT SIGNALS		OUTPUT p-p	Gain
	V1 (p-p)	V2 (p-p)		
1				
2				
3				
4				
5				

CALCULATIONS:

Calculated Gain:

Lab Session 03

OBJECTIVES


To investigate the Operation of Inverting Integrator

EQUIPMENT REQUIRED:

Protoboard
741 Opamps
Resistors, Capacitors
Digital Multimeter
Function Generator
Oscilloscope

THEORY:

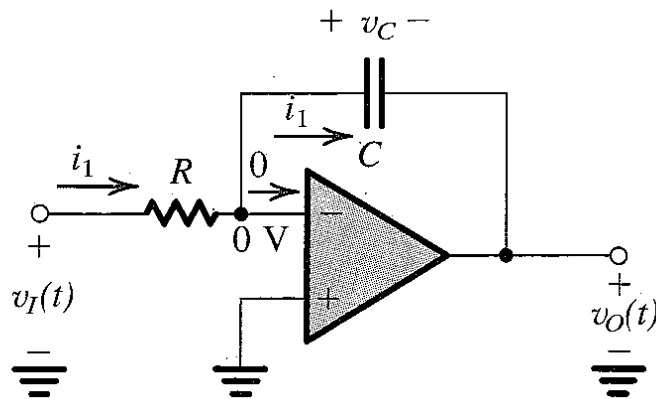By placing the capacitor in the feedback path, and resistor at the input realizes the mathematical operation of integration.



OBSERVATIONS:

S. No	Frequency	Input (p-p)	Output (p-p)	Gain
1	1k			
2				
3				
4				
5	10k			
6				
7				
8				
9	100k			
10				
11				
12				

CALCULATIONS:

The integrating frequency according to the values of C & R is:

Lab Session 04

OBJECTIVES

To investigate the Operation of BJT Current Mirror.

EQUIPMENT REQUIRED:

Protoboard
Q2N2222 BJT npn transistors
Resistors, Capacitors
Digital Multimeter
Function Generator
Oscilloscope
Connecting wires

THEORY:

The basic BJT Current Mirror is shown in figure. Neglecting base current, the reference current I_{REF} is passes through the diode connected transistor Q_1 , & thus produces corresponding voltage V_{be} , which in turn is applied between base & emitter of Q_2 . If Q_2 is matched to Q_1 , then the collector current of Q_1 is equal to that of Q_2

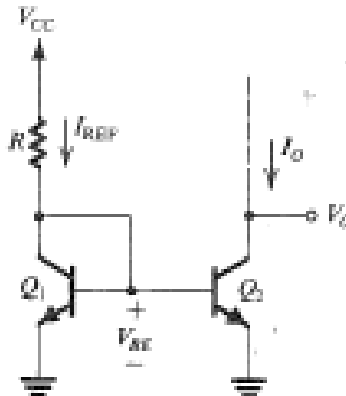


FIGURE 1

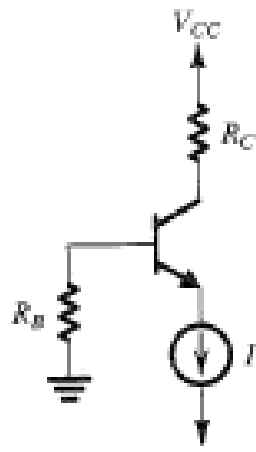


FIGURE 2

PROCEDURE:

- Implement the circuit given in figure 2, using current source in figure 1.
- Vary the potentiometer and observe changes in I_{ref} and I_o

OBSERVATIONS:

S. No	I_{ref}	I_o
1		
2		
3		
4		
5		
6		
7		
8		

CALCULATIONS:

Lab Session 05

OBJECTIVES


To illustrate the operation of current source implemented using BJT, with Base-Current Compensation.

EQUIPMENT REQUIRED:

Protoboard
Q2N2222 BJT npn transistors
Resistors, Capacitors
Digital Multimeter
Function Generator
Oscilloscope
Connecting wires

THEORY:

Figure shows a bipolar current mirror with a current transfer ratio that is much less dependent on β than that of simple current mirror. The reduced dependence is achieved by using transistor Q3

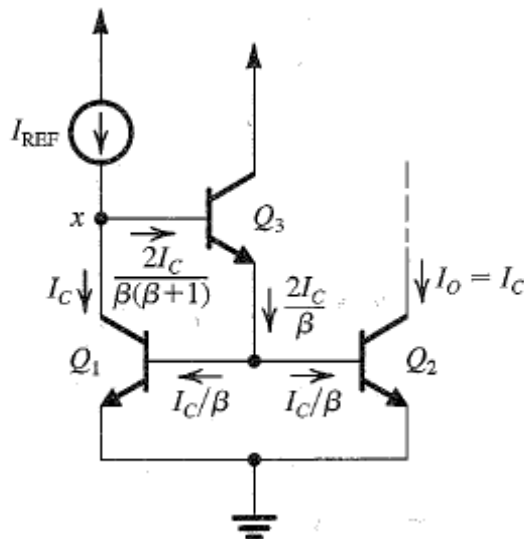

PROCEDURE:

- Implement the circuit in figure 2 of previous lab session using above current source, using potentiometer in place of I_{ref}
- Vary potentiometer & observe readings for I_{ref} & I_o

OBSERVATIONS:

S. No	I_{ref}	I_o
1		
2		
3		
4		
5		
6		
7		
8		

CALCULATIONS:

Lab Session 06

OBJECTIVES


To illustrate the operation of BJT Differential Pair
As a Switch
As an Amplifier

EQUIPMENT REQUIRED:

Protoboard
Q2N2222 BJT npn transistors
Resistors, Capacitors
Digital Multimeter
Function Generator
Oscilloscope
Connecting wires

THEORY:

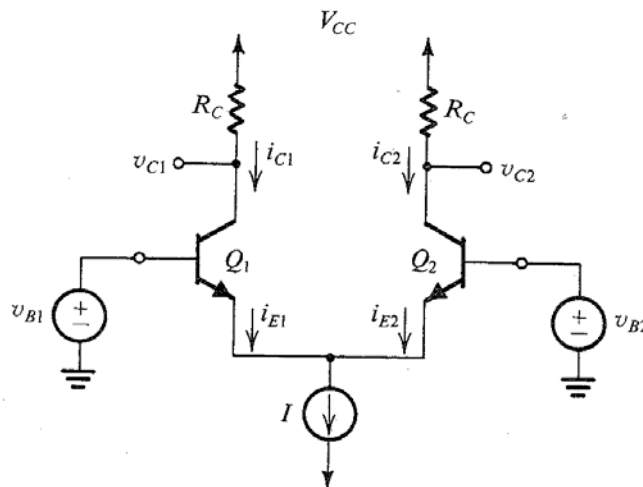
It consists of two matched transistors, Q_1 & Q_2 , whose emitters are joined together and biased by constant current source I . It is essential that, collector circuits be such that Q_1 & Q_2 never enter saturation.



OBSERVATIONS:

S.NO	V B1	VB2	VB1-VB2	Vc1	Vc2	Vc1-Vc2
1						
2						
3						
4						
5						
6						
7						
8						

RESULTS:

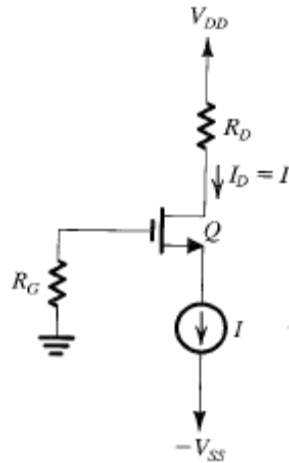

PROCEDURE:

- Implement the circuit in figure 2 using MOS Wilson current Mirror as that in figure 1, using potentiometer in place of Iref
- Vary potentiometer & observe readings for Iref & I_o

OBSERVATIONS:

S. No	Iref	I _o
1		
2		
3		
4		
5		
6		
7		
8		

CALCULATIONS:

Lab Session 08

OBJECTIVES


To illustrate the operation of Common Source Amplifier and also determine phase shift between input and output.

EQUIPMENT REQUIRED:

Protoboard
Q2N2222 BJT npn transistors
Resistors, Capacitors
Digital Multimeter
Function Generator
Oscilloscope
Connecting wires

THEORY:

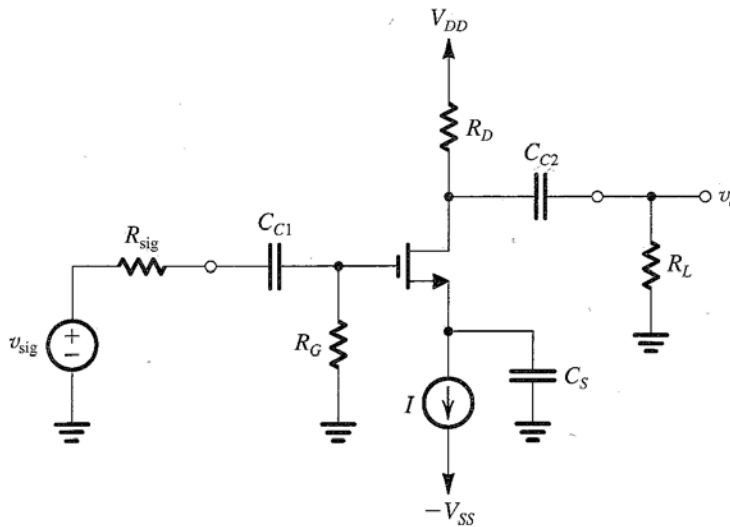A Common Source Amplifier or Grounded Source Configuration is shown in figure. To establish a signal ground, or ac ground, a large capacitor is connected between source & ground. The signal current bypasses the output resistance of the current source & is called a bypass Capacitor. C_{C1} is known as Coupling Capacitor, & acts as a perfect short circuit at all signal frequencies of interest.



OBSERVATIONS:

S.No	Frequency	Input (p-p)	Output (p-p)	Gain
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				

CALCULATIONS:

Calculated Gain:

Lab Session 09

OBJECTIVES


To illustrate the operation of Common Gate Amplifier.

EQUIPMENT REQUIRED:

- Protoboard
- MOSFET
- Resistors, Capacitors
- Digital Multimeter
- Function Generator
- Oscilloscope
- Connecting wires

THEORY:

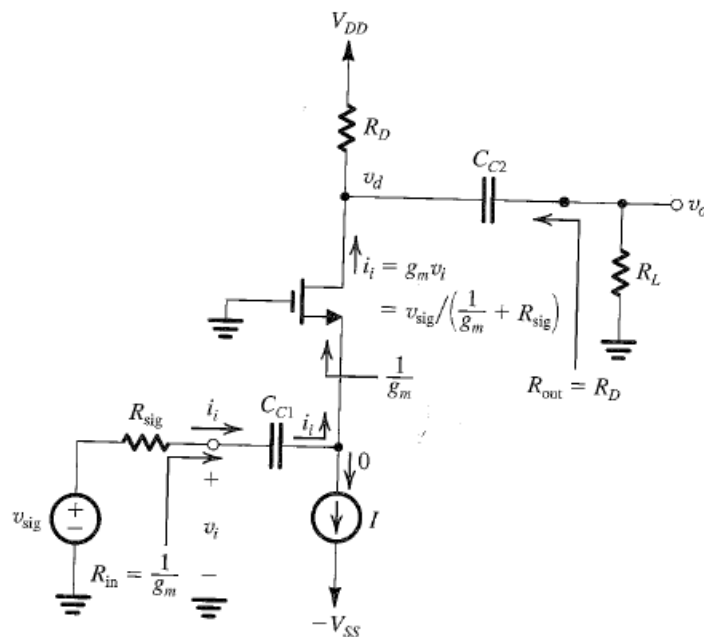By establishing a signal ground on the MOSFET gate terminal, a circuit configuration called Common Gate is obtained. The input is applied to the source and output is taken at the drain terminal, with gate being the common terminal between input & output ports.



OBSERVATIONS:

S.No	Frequency	Input (p-p)	Output (p-p)	Gain
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				


CALCULATIONS:

Calculated Gain:

Lab Session 10

PROJECT # 1

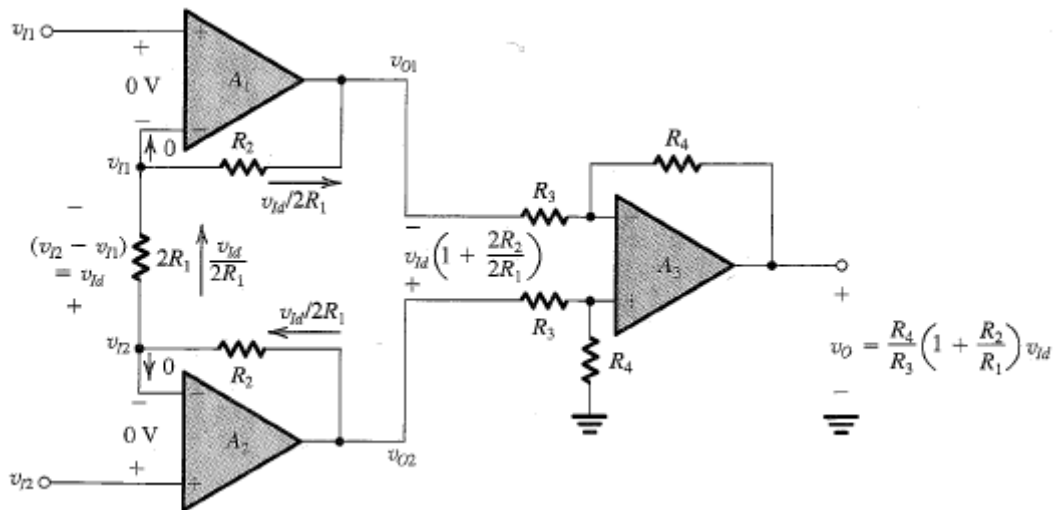To illustrate the operation of Instrumentation Amplifier




Lab Session 11

PROJECT # 2

To illustrate the operation of BJT Cascode Configuration and thus find:

1. Gain
2. Frequency Response

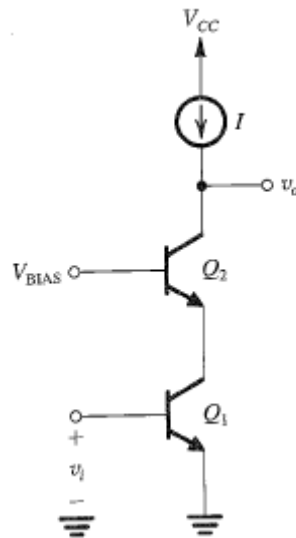

Lab Session 12

PROJECT # 3

To illustrate the operation of Common Drain Amplifier

